



Welcome to The Hardware Lab!

Fall 2016

Lab 4: Finite State Machine

Prof. Chun-Yi Lee

**Department of Computer Science
National Tsing Hua University**

Verilog Lab 4

- **Five basic questions (50%)**
 - Demonstration on **11/17/2016 (Thu), in class**
- **Lab 4 report (30%)**
 - **Circuit or block diagram, and FSM state transition diagram** of your design, **and explain how it works**
 - Answer the questions listed in the handout (if any)
 - Contribution of each team member
 - What you have learned from Lab 4
- **Two optional questions (20%)**
 - Challenge it if you have extra time
 - Include in your Lab 4 report if you can make it
 - **Describe your design and how it works**

Verilog Lab 4 Rules


- You can use **ANY** modeling techniques
- Demonstrate your work by **waveforms (Q1~Q5, OQ2) and FPGA (OQ1)**
- Please follow the **module names** and **I/O ports** of the provided templates
 - Submit **only one testbench file** and **one design file**
 - **Avoid commenting out** modules in your submitted Verilog files
 - **Please keep in mind that we will deduct points if the module names and I/O port mismatch with the template**
- If not specifically mentioned, we assume the following SPEC
 - **CLK** is **positive edge triggered**
 - Reset the Flip-Flops when **RESET == 1'b0**

Verilog Lab 4 Submission

- **Demonstration, code and report** submission due date & time:
5:30pm, 11/17/2016 (Thu)
This is a HARD deadline
- Please submit your report and Verilog codes to **ILMS**
 - Format: **Lab4_Team1_Codes.v, Lab4_Team1_Tb.v, Lab4_Team1_Report.pdf**
 - **We will deduct points if the submitted files mismatch the requirements**
 - **Please don't uncomment the modules in the template file**
- We will test your codes by our own testbench


Question 1

- Please implement the following FSM
 - **Green** represents input, while **red** represents output
 - Output your **current state** as well
 - When RESET == 1'b0, State = S0

 


Question 2

- Please implement the following FSM
 - **Green** represents input, while **red** represents output
 - Output your **current state** as well
 - When RESET == 1'b0, State = S0

 


Question 3

- **Mealy machine sequence detector**
 - 1-bit input **In** and 1-bit output **Dec**
 - When the four bit sequence is either **1001**, **Dec** is set to 1
 - Redetect the sequence **every four bits**
 - Please draw your state diagram in your report

 

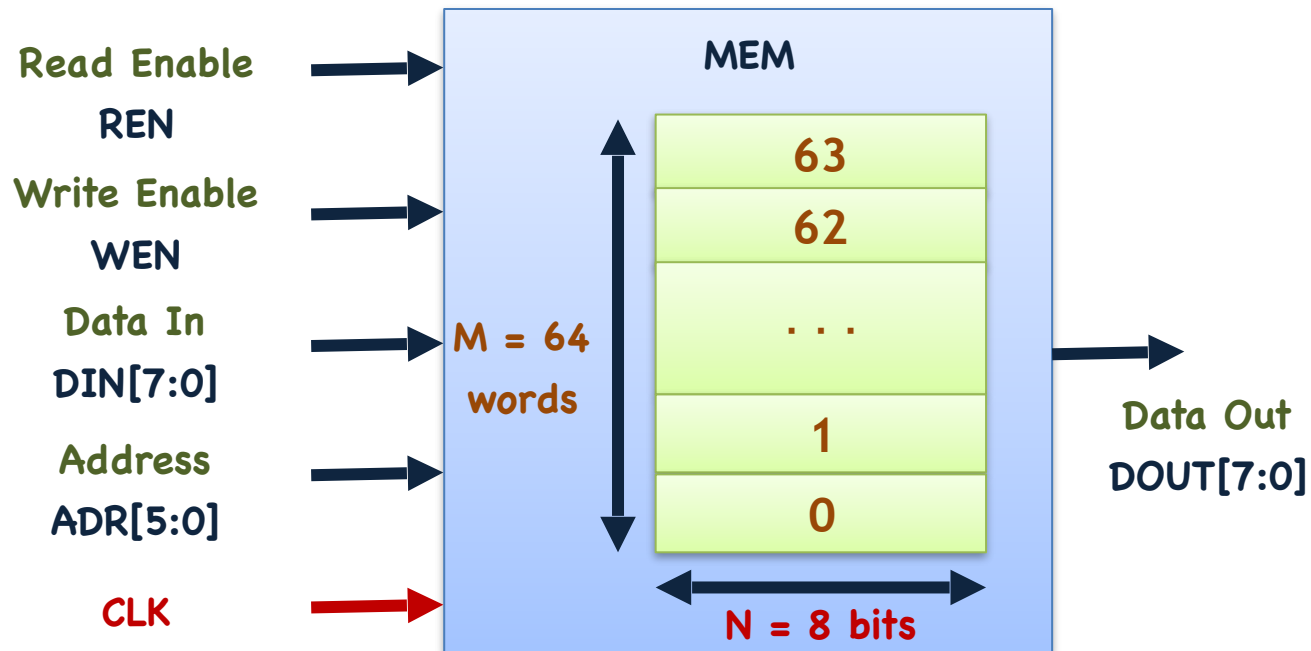
Question 4

- Assume that we have a **64 x 8** memory array **MEM**
 - **M** = 64, **N** = 8
 - **Inputs:** CLK, REN, WEN, ADDR[5:0], DIN[7:0]
 - **Outputs:** DOUT[7:0]




Question 4 Specification

- Specification
 - When $WEN == 1'b0$, write DIN to $MEM[ADDR]$
 - When $REN == 1'b0$, output $MEM[ADDR]$ to $DOUT$; otherwise $DOUT = 8'd0$
 - REN and WEN won't be zero at the same time. **If both are 0, do only the read operation**
 - **MEM** does not need to be reset

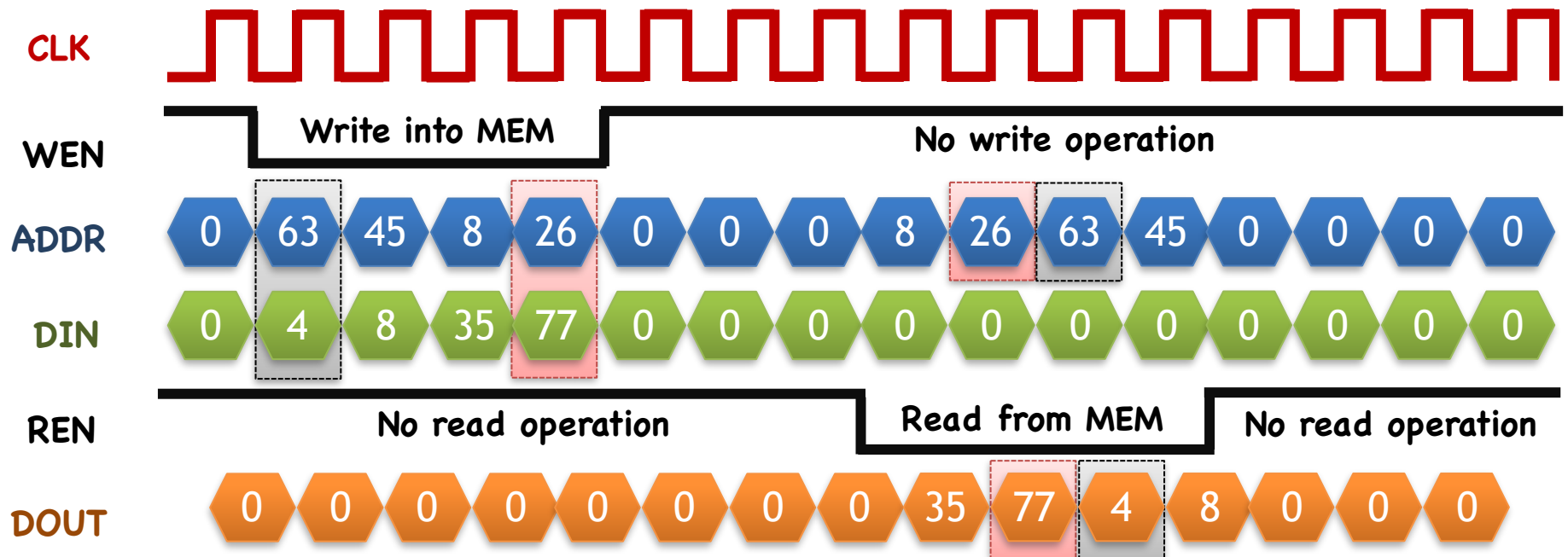

 
Question 5

- **Traffic light controller** for highway (HW) and local road (LR) intersection
- **HW** has higher priority and should be green as long as possible
- **LR** has a sensor to detect cars on it. When a car is sensed, LR turns green shortly
- Green light is **at least 25** clock cycles and yellow light is **5** clock cycles
- **Input:** **CLK**, **RESET**, LR_has_Car; **Output:** HW_light[2:0], LR_light[2:0]
 - HW_light & LR_light: bits [2:0] represent **Red**, **Yellow**, and **Green**, respectively



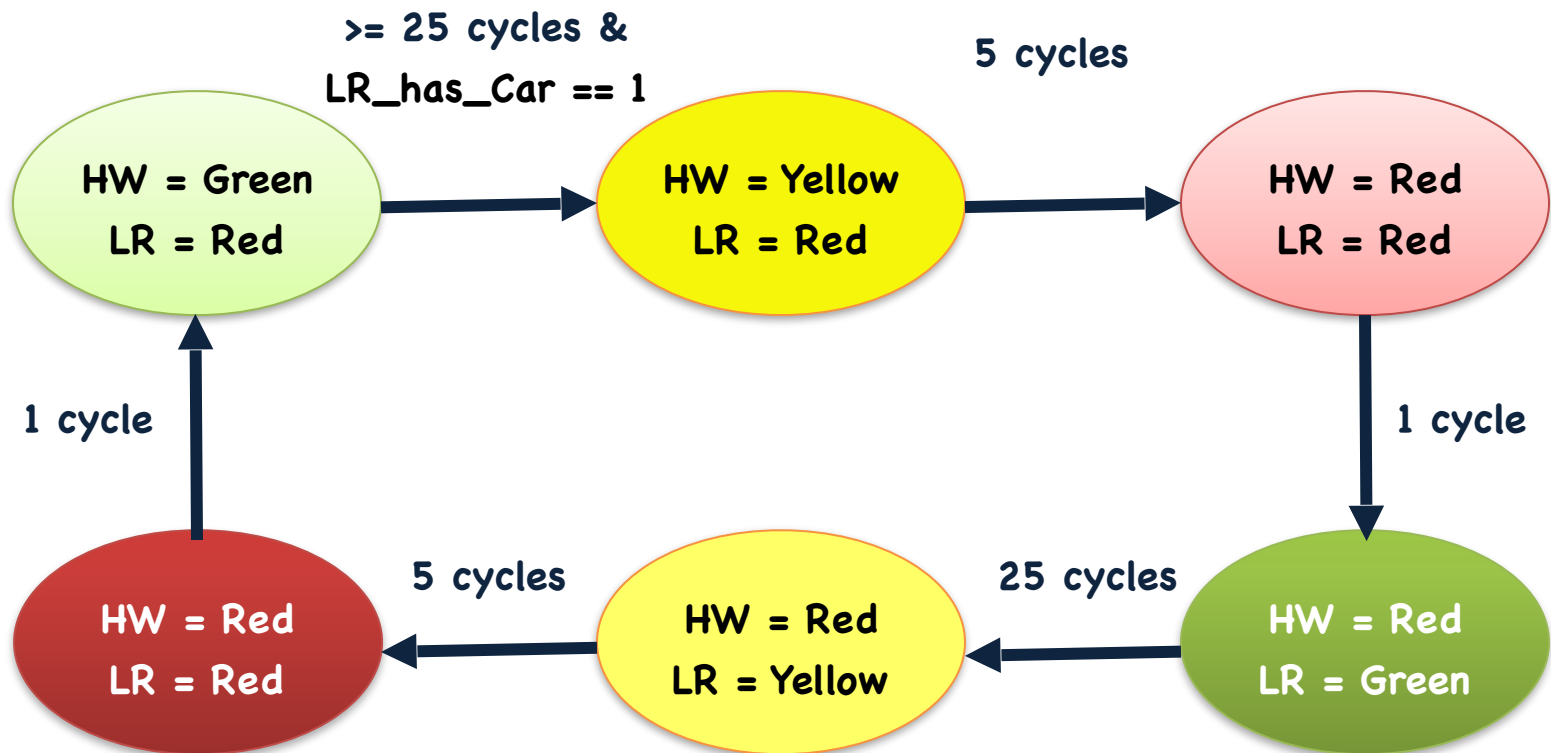
Question 5 Finite State Machine

- **Traffic light controller** Finite State Machine
- **Please complete the FSM in your report** (some arrows are removed intentionally)



Optional Question 1

- Please design a stopwatch and display it on your 7-segment display
- The four digits represent:
 - Digit[3]: Minutes
 - Digit[2:1]: Seconds
 - Digit[0]: 0.1 Seconds
 - Dot: Separates the third and fourth digits
- Use a push-button (**UP button, T18**) with debounce to start counting up
- Use another push-button (**RIGHT button, T17**) with debounce to reset
- Three FSM states: **RESET, WAIT, COUNT**
 - **please draw a state transition diagram in your report**

 

Optional Question 2

- Design a 4-bit Ping-Pong Counter with MAX and MIN
 - Input: **CLK, RESET, Enable, FLIP, MAX[3:0], MIN[3:0]**
 - Out: **0,1,2,...,7,8,9,8,7,...,2,1,0,1,2,...**
 - Direction: **0,0,0,...,0,0,0,1,1,...,1,1,1,0,0,...**
 - In the above example, MAX is 9 and MIN is 0



Optional Question 2 SPEC

- **4-bit Ping-Pong Counter SPEC**
 - When **RESET** == 1'b0, the counter resets its value to **MIN**
 - When **Enable** == 1'b1, the counter begins its operation. Otherwise, the counter holds its current value
- **MAX and MIN**
 - **MAX** and **MIN** values are the maximum and minimum values for the counter
 - **MAX** >= **MIN**. Otherwise, counter holds its current value
 - When counter > **MAX** or counter < **MIN**, counter holds its current value
- **FLIP**
 - When **FLIP** == 1'b1, counter flips its direction
 - Flip is **only one cycle** in length

Thank you for your attention!



*The first Starbucks at Seattle, Washington, USA
This picture is taken by Chun-Yi Lee himself, who is also a fan of photography